

HM-7 users might be interested to know that by installing a 4.7mfd across the 220 ohm emitter resistor inside the HM 7 built in pre-amp will increase audio output.

### Schematic diagram of IC-HM7

